
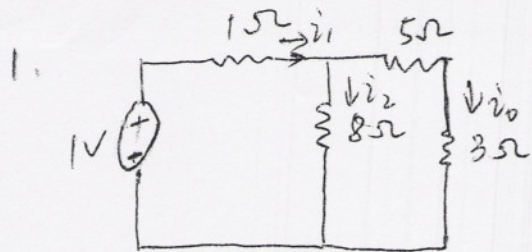


ch 4

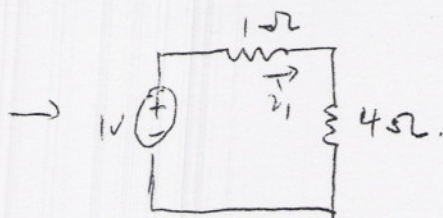

$$i_0 = i_1 - i_2$$

$$i_0 = 0.1 \text{ A}$$




$$i_1 = \frac{1}{5} = 0.2 \text{ A}$$

$$i_2 = 0.1 \text{ A}$$

Linear: 10V \rightarrow $i_0 = 1 \text{ A}$

2. $i_{2\Omega} = 0.25 \text{ A}$, $V_0 = 2(0.25) = 0.5 \text{ V}$

Linear, 1mA $V_0 = 0.5 \mu\text{V}$

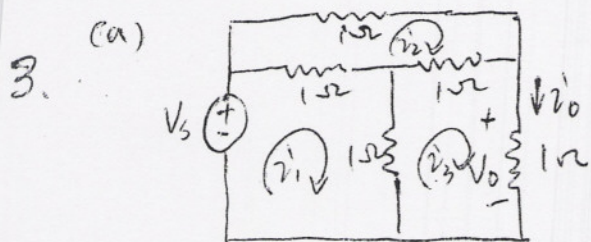

$$\begin{cases} 1 + 2i_1 - i_2 - i_3 = 0 \\ -i_1 - i_2 + 3i_3 = 0 \\ -i_1 + 3i_2 - i_3 = 0 \end{cases} \Rightarrow \begin{cases} i_1 = 1 \text{ A} \\ i_2 = -1.5 \text{ A} \\ i_3 = 0.5 \text{ A} \end{cases}$$


$$i_0 = i_3 = 0.5 \text{ A}$$

$$V_0 = 1 \cdot (0.5) = 0.5 \text{ V}$$

(b) Linear, $i_0 = 5 \text{ A}$ $V_0 = 5 \text{ V}$

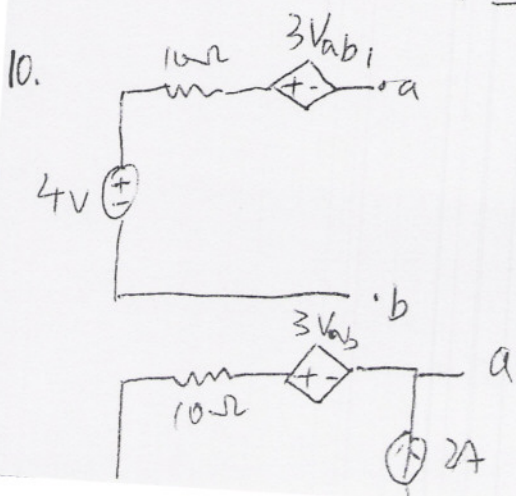(c) $V_s = 10 \text{ V}$, $i_0 = 0.5 \text{ A}$



$$V_0 = i_0 R = 0.5 \times 10 = 5 \text{ V}$$



$$V_{ab1} = 4 - 3V_{ab1} \Rightarrow V_{ab1} = 1 \text{ V}$$

$$V_{ab2} = 2 \times 10 - 3V_{ab2} \Rightarrow V_{ab2} = 5 \text{ V}$$

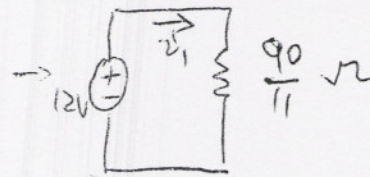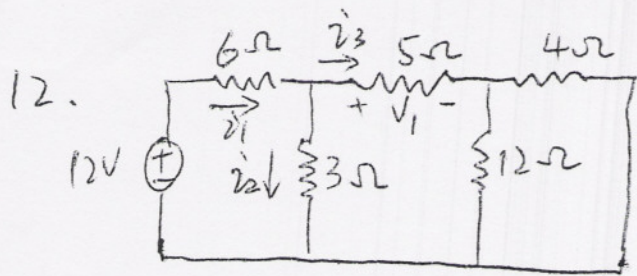
$$V_{ab} = V_{ab1} + V_{ab2} = 1 + 5 = 6 \text{ V}$$



$$i_1 = \frac{12}{90} \times 11 = \frac{22}{15} \text{ A}$$

$$i_3 = \frac{3}{11} i_1 = 0.4 \text{ A}$$

$$V_1 = 2 \text{ V}$$


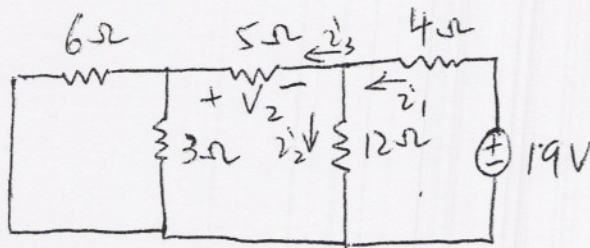


$$i_1 = \frac{19}{160} \times 19 = \frac{361}{160} \text{ A}$$

$$i_3 = \frac{12}{19} i_1 = \frac{228}{160} \text{ A}$$



$$V_2 = -\frac{228}{160} \times 5 = -7.125 \text{ V}$$
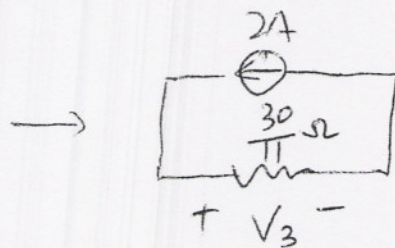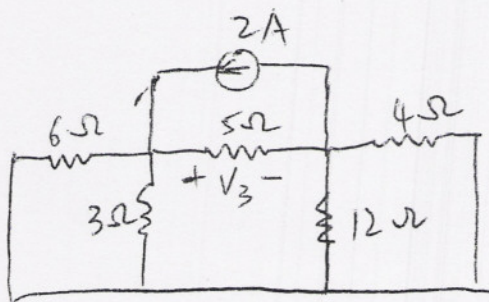
$$V_3 = 2 \left(\frac{30}{11} \right) = 5.455 \text{ V}$$



$$V = V_1 + V_2 + V_3 = 2 + 7.125 + 5.455 = \boxed{14.57 \text{ V}}$$


24

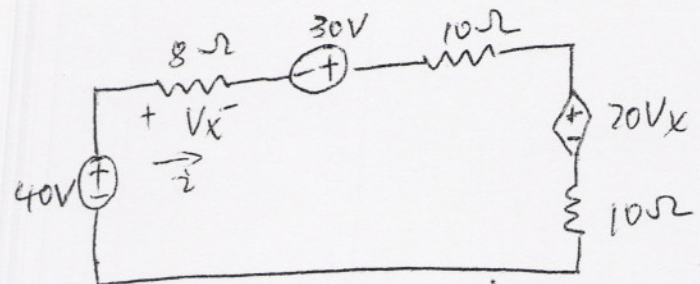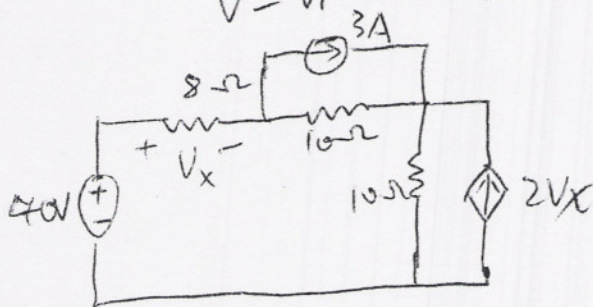


$$\text{KVL, } 40 - 8i + 30 - 10i - 20V_x - 10i = 0$$

$$V_x = 8i, \quad i = \frac{70}{188}, \quad V_x = 8 \times \frac{70}{188} = \boxed{2.99 \text{ V}}$$


27.

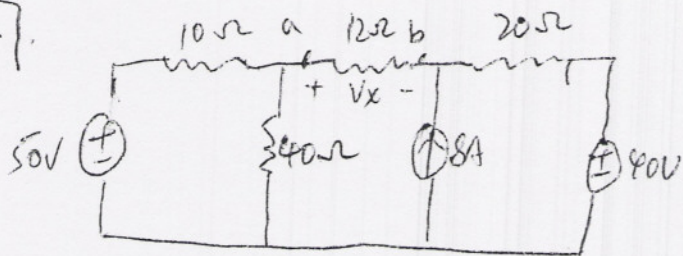


(1)

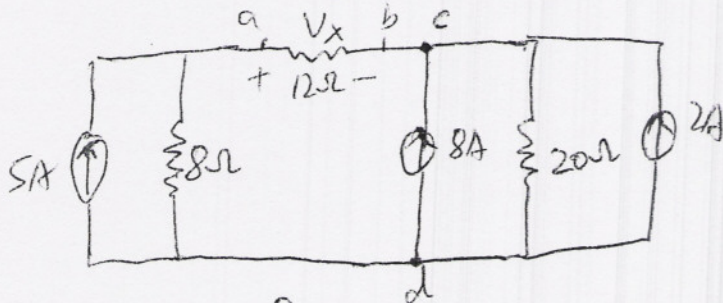




(2)

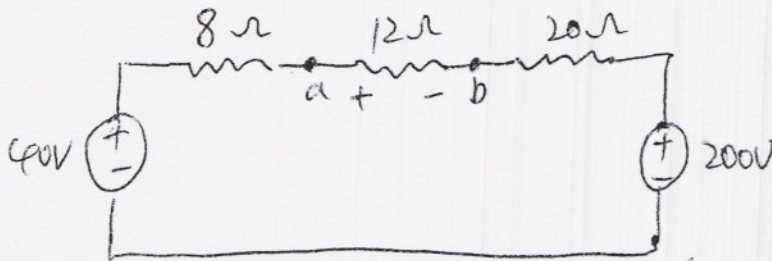


28.

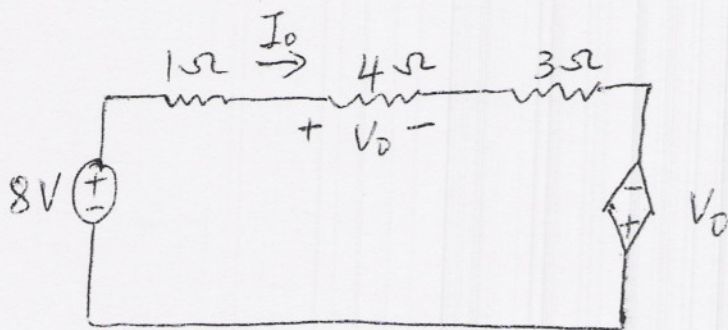

33. (a)

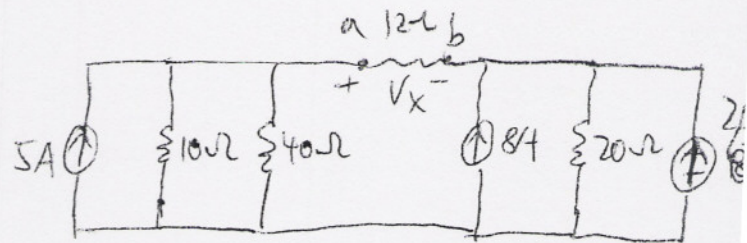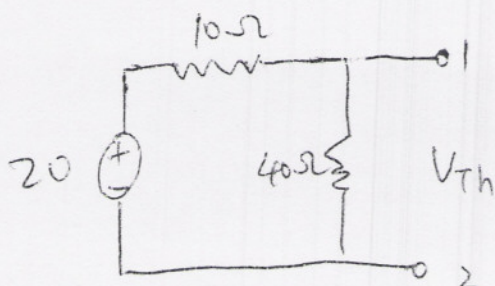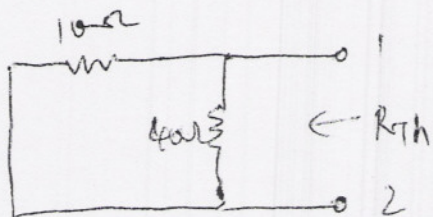

(2)

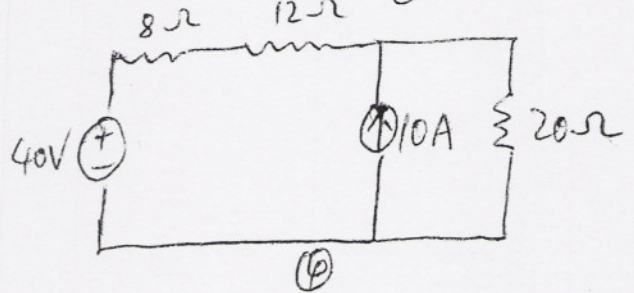

(1)

KVL:

$$V_{ab} = \frac{12}{8+12+20} (40-200) = \boxed{-48V}$$

$$V_0 = 4I_0$$

KVL:


$$8 - I_0 - 4I_0 - 3I_0 + 4I_0 = 0$$

$$\boxed{I_0 = 2A}$$

$$R_{Th} = \frac{10 \times 40}{10+40} = \boxed{8\Omega}$$

$$V_{Th} = \frac{40}{10+40} \times 20 = \boxed{16V}$$


44. (a)

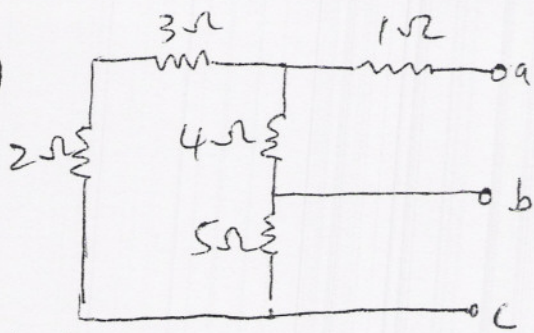

$$R_{Th} = R_{2+3+5} \parallel R_4 + R_1$$


$$= 3\Omega$$

Source Transmission

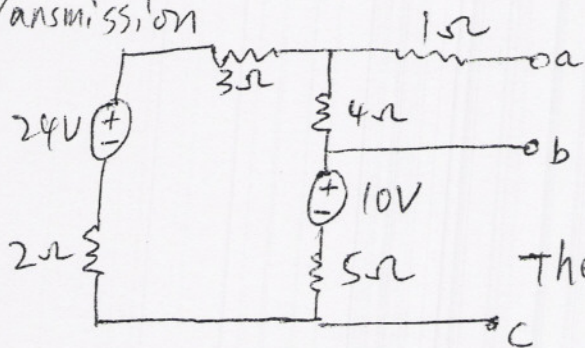

$$V_{Th} = V_{ab} = (24 - 10) \cdot \frac{4}{3 + 4 + 5 + 2}$$


Thevenin equivalent =

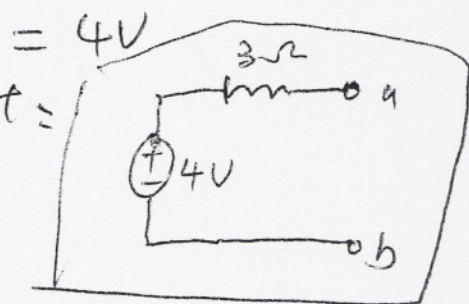


(b)

$$R_{Th} = R_{bc} = R_{2+3+4} \parallel R_5 = 3.21\Omega$$


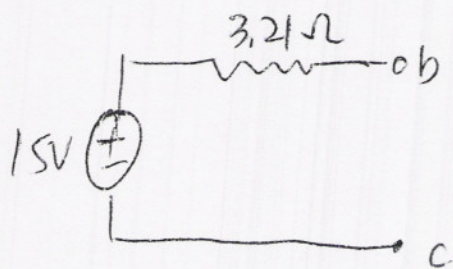
$$V_{Th} = V_{bc} = (24 - 10) \left(\frac{5}{3 + 4 + 5 + 2} \right) + 10 = 15V$$



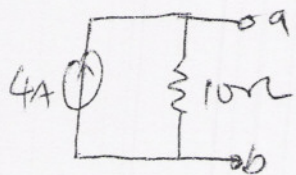46. $R_N = (10 + 10) \parallel 20 = 10\Omega$




47

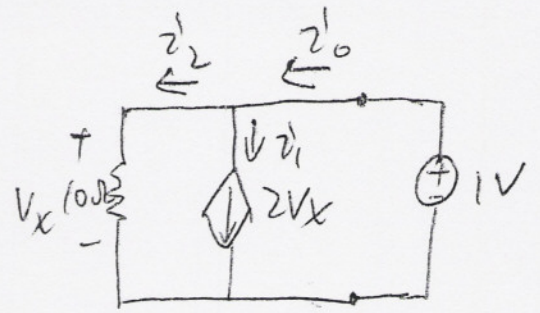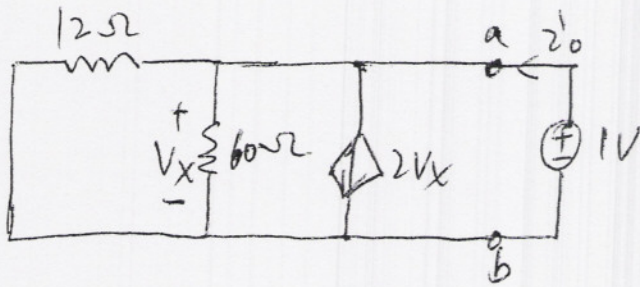

$$V_x = 1V, \quad i'_1 = 2V_x = 2A, \quad i'_0 = i'_1 + i'_2 = 2.1A$$

$$i'_2 = \frac{V_x}{10} = 0.1A$$
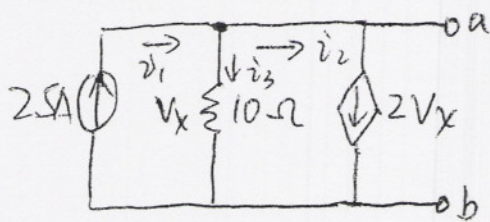
$$R_{Th} = R_N = \frac{1}{2.1} = \boxed{476.2 \text{ m}\Omega}$$



$$i_1 = 2.5, \quad i_2 = 2V_x$$

$$i_3 = i_1 - i_2 = 2.5 - 2V_x$$

$$V_x = 10i_3, \quad V_x = \frac{2.5}{21} = \boxed{1.19V}$$

$$V_{Th} = V_x = 1.19V$$

$$I_N = \frac{V_{Th}}{R_{Th}} = \boxed{2.5A}$$

