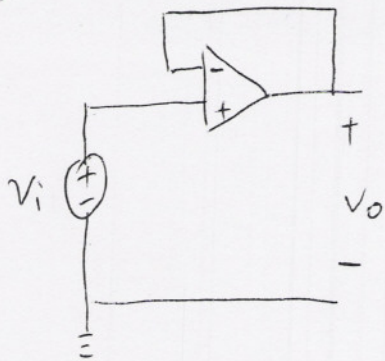


5. ch5




$$V_i - V_d = V_o$$

$$V_o = AV_d$$

$$V_i = \left(\frac{A+1}{A} \right) V_o$$

$$\frac{V_o}{V_i} = \frac{A}{A+1} = \boxed{0.999999}$$

Answer

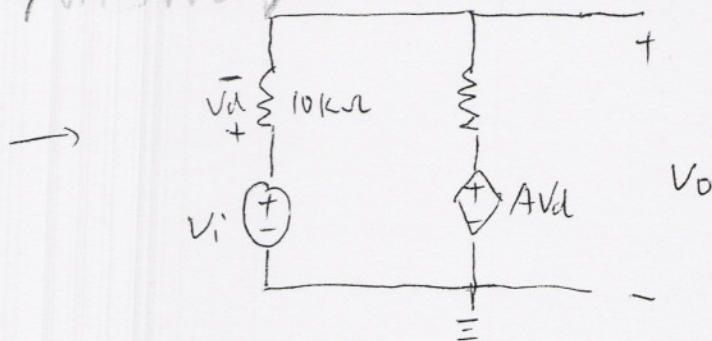


8. a) Ideal op Amp


$$V_1 = V_2$$

$$V_1 = V_2 = 0, \quad V_o = -2000 \times 0.001 = \boxed{-2V}$$
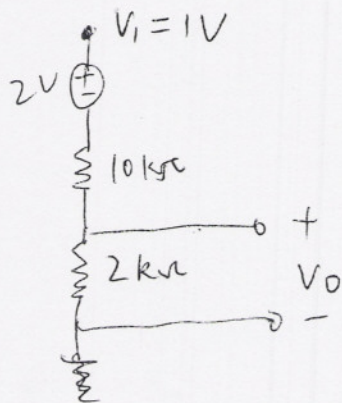
$$b) \quad V_1 = V_2 = 1V, \quad V_o = (-1) \left(\frac{2}{12} \right) = \frac{1}{6} V = \boxed{167mV}$$




10.

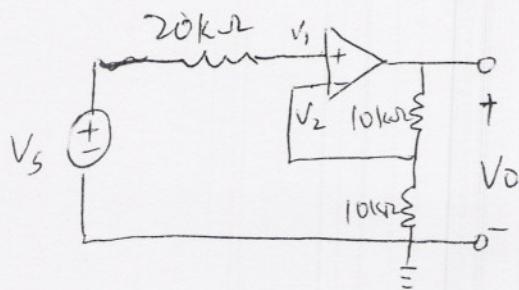

$$V_2 = \frac{V_o}{2}, \quad V_1 = V_2 = V_s$$

$$\frac{V_o}{V_s} = \boxed{2}$$

15.

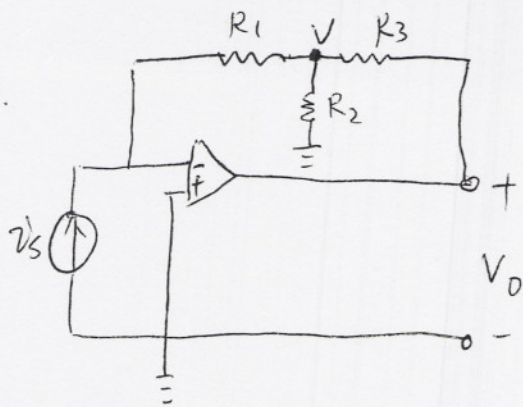

$$(a) \quad v_s = \frac{V}{R_2} + \frac{V - V_0}{R_3}$$

$$V = -v_s R_1$$

$$v_s = -\frac{v_s R_1}{R_2} + \frac{-v_s R_1 - V_0}{R_3}$$


$$\frac{V_0}{v_s} = \left[-\left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right) \right]$$

(b)

$$\frac{V_0}{v_s} = -\left(20\text{k}\Omega + 40\text{k}\Omega + \frac{(20\text{k}\Omega)(40\text{k}\Omega)}{25\text{k}\Omega} \right)$$

$$= \boxed{-92\text{k}\Omega}$$

21.

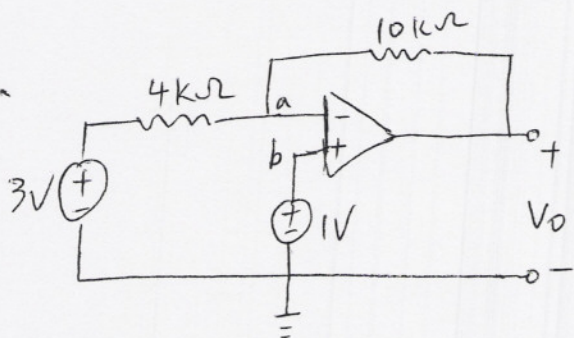

$$\frac{V_a - V_0}{10\text{k}\Omega} = \frac{3 - V_a}{4\text{k}\Omega}$$

$$\Rightarrow V_0 = 3.5V_a - 7.5$$

$$V_a = V_b = 1\text{V}$$

$$V_0 = \boxed{-4\text{V}}$$

$$34 \quad V_{in} = \frac{R_3}{R_3 + R_4} V_0$$

$$v_+ = v_- = 0$$

~~$$V_{in} = V_0$$~~

$$\frac{V_1 - V_{in}}{R_1} + \frac{V_2 - V_{in}}{R_2} = 0$$


$$\frac{V_1 - \frac{R_3}{R_3 + R_4} V_0}{R_1} + \frac{V_2 - \frac{R_3}{R_3 + R_4} V_0}{R_2} = 0$$

$$\Rightarrow V_0 = \left[\left(1 + \frac{R_4}{R_3} \right) \frac{(V_1 R_1 + R_1 V_2)}{(R_1 + R_2)} \right]$$

$$37. \quad V_0 = - \left[\frac{30}{10} (1) + \frac{30}{20} (2) - \frac{30}{30} (3) \right]$$

$$= \boxed{-3V.}$$

54.

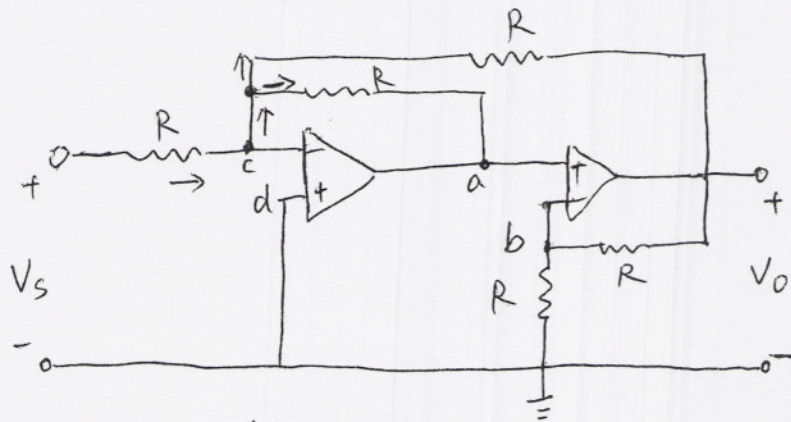

$$V_a = V_b = \frac{V_0}{2}$$

$$V_c = V_d = 0$$

$$\frac{0 - V_s}{R} = \frac{V_a - 0}{R} + \frac{V_0 - 0}{R}$$

$$\frac{-V_s}{R} = \frac{V_a}{R} + \frac{V_0}{R}$$

$$\boxed{\frac{V_0}{V_s} = -\frac{2}{3}}$$