

CHAPTER 3

116.

$$H = I/2\pi r = 50/0.2\pi = 79.6\text{A/m}$$

ANSWER (C)

516.

The path length for Leg B is  $d$ , and the path length for Leg C is  $3d$ . Thus, the flux will divide between Legs B and C in the ratio of 1:3. Therefore,  $1/4$  of the total flux will be in Leg C and  $3/4$  will be in Leg B.

$$\Phi_{PC} = 1/4 \times 3.0 \times 10^{-3} = 0.75 \times 10^{-3}\text{Wb}$$

ANSWER (B)

CHAPTER 4

$$\begin{aligned} V_{sec} &= I_{line} \left( \frac{0.78 + j0.052}{1,000 \text{ ft}} \right) (200 \text{ ft}) + V_{load} + I_{line} \left( \frac{0.78 + j0.052}{1,000 \text{ ft}} \right) (200 \text{ ft}) \\ &= 240 \angle 0^\circ + (2)(30 \angle 0^\circ) \left( \frac{1}{5} \right) (0.78 + j0.052) \\ &= 249.4 \angle 0.143^\circ \text{ V} \end{aligned}$$

133.  $|V_{sec}| = 249.4 \text{ V}$

ANSWER (B)

135.

$$P_{load} = 8,000 \text{ kW}$$

$$P.F. = 0.80$$

$$S_{Zoad} = 8,000\text{kW} / 0.80 = 10,000\text{kVA}$$

$$Q_{Zoad} = \sqrt{10,000^2 - 8,000^2} = 6,000 \text{ kvar}$$

$$S_{new} = 8,000\text{kW} / 0.95 = 8421\text{kVA}$$

$$Q_{new} = \sqrt{8,421^2 - 8,000^2} = 2,630 \text{ kvar}$$

$$Q_{cap} = Q_{Zoad} - Q_{new} = 6,000 - 2,630 = 3,370\text{kvar}$$

ANSWER (B)

508.

For this unbalanced load,  $I_A + I_B + I_N = 0$

$$\text{Also, } V_{\phi N} = V_{\phi\phi} / \sqrt{3} = 13.2 / 1.732 = 7.62 \text{ kV}$$

$$|I_A + I_B| = |-I_N| = \left| \frac{200 + j100}{7.62 \angle 0^\circ} + \frac{200 + j100}{7.62 \angle 120^\circ} \right| = 29.3 \text{ A}$$

ANSWER (D)

509.

The system is initially ungrounded (the utility neutral is disconnected from ground). Connecting Corner A of the delta to ground will therefore have no effect on the relative phase voltages and  $V_{BG} = V_{BA} = 13.2 \text{ kV}$ .

ANSWER (C)

510.

$$I_c = 500 \text{ kVA} / 13.2 \text{ kV} = 37.9 \text{ A}$$

ANSWER (C)

511.

The system is balanced.

$$V_{an} = \frac{12.5}{\sqrt{3}} \angle -30^\circ + \frac{70 \angle -20^\circ}{1,000} (5 + j10) = 7.48 \angle -24.2^\circ$$

$$|V_{ab}| = 7.48 \sqrt{3} = 12.95 \text{ kV}$$

ANSWER (C)

## CHAPTER 5

123.

The power input to the speaker is  $V^2/R = (30)^2/8 = 900/8 = 112.5 \text{ W}$ . The speaker output is  $(112.5 \text{ W})(0.15) = 17 \text{ W}$ .

ANSWER (B)